

[6352]-157R

**S.E. (Computer Science and Engineering) (Data Science)**  
**DIGITAL ELECTRONICS AND LOGIC DESIGN**  
**(2019 Pattern) (Semester - III) (210644)**

Time : 2½ Hours]

Instructions to the candidates :

[Max. Marks : 70

- 1) Answer Q.1 or Q.2, Q.3 or Q.4, Q.5 or Q.6, Q.7 or Q.8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right indicate full marks.
- 4) Assume suitable data, if necessary.

- Q1) a) Distinguish between combinational and sequential switching circuits also write examples of both. [6]  
 b) Convert following flip flops [6]  
 i) SR to JK  
 ii) JK to D  
 c) Draw and explain 4-bit asynchronous up-counter using JK flip flop. Also draw the necessary timing diagram. [6]  
 OR  
 Q2) a) What is MOD counter? Design MOD 7 counter using IC 7490. [6]  
 b) With neat diagrams explain the working of the following types of shift Registers [6]  
 i) Serial-in, serial-out  
 ii) Parallel-in, serial-out  
 c) What do you mean by excitation table of flip flop? Write the excitation table of [6]  
 i) SR flip flop  
 ii) J-K flip flop  
 Q3) a) Draw an ASM chart and state table of a 2 bit up-down counter having a mode control input. [6]  
 M = 1 Up counting M = 0 down counting  
 b) What is an ASM Chart? Name the elements of an ASM chart and define each of them. [6]

P.T.O.

- c) Implement following Boolean function using PAL [5]  
 $F1 = \sum m(0, 2, 4, 6, 8, 12)$   
 $F2 = \sum m(2, 3, 8, 9, 12, 13)$   
 $F3 = \sum m(1, 3, 4, 6, 9, 11, 12, 14, 15)$   
 OR

- Q4) a) Draw a block diagram of the PLA device and explain. [6]  
 b) Implement BCD to Gray code converter using PAL. [6]  
 c) What is the difference between PAL and PLA? [6]

3

- Q5) a) What is the advantage of open collector output? Justify your answer with suitable circuit. [6]  
 b) Compare TTL and CMOS logic family. [6]  
 c) What is logic family? Give the classification of logic family and also write important characteristics of CMOS. [6]

OR

- Q6) a) Draw and explain the circuit diagram of CMOS inverter. [6]  
 b) Define the following terms and mention the standard values for TTL logic Family [6]  
 i) Fan-out  
 ii) Power Dissipation  
 iii) Propagation Delay  
 c) With the help of a neat diagram, Explain the working of two-input TTL NAND gate. [6]

- Q7) a) What is system bus? Draw microprocessor bus structure and explain in brief. [6]  
 b) Write a short note on following with respect to microprocessor. [6]  
 i) Address Bus  
 ii) Data Bus  
 iii) Control Bus  
 c) Explain the Memory organization of the microprocessor. [5]  
 OR

- Q8) a) What is Microprocessor? List different applications of Microprocessor. [6]  
 b) Write a short note on ALU IC 74181. [6]  
 c) With the help of a block diagram explain the fundamental units of a Microprocessor. [5]

▽▽▽▽

[6352]-157R